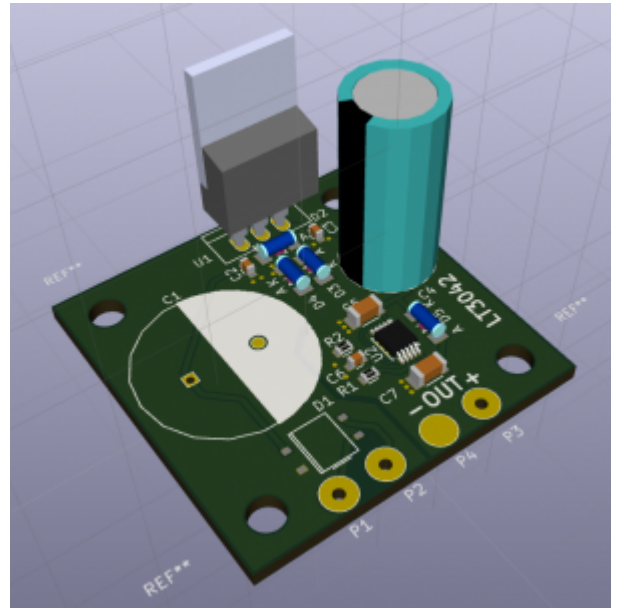


Ultra Low Noise Linear Power Supply, using LT3042

Small power regulator pcb, with AC inputs and DC output.

- Output voltage: 0-15V
- Output current: max. 200mA
- Input voltage: max. 20VAC



Schematic

[rauscharmest-netzteil-5v.pdf](#)

KiCad project

[uln-power-supply-kicad.7z](#)

From:

<http://www.zeilhofer.co.at/wiki/> - Verschiedenste Artikel von Karl Zeilhofer

Permanent link:

<http://www.zeilhofer.co.at/wiki/doku.php?id=uln-power-supply&rev=1455209362>

Last update: **2016/02/11 17:49**

